

B.M.S College of Engineering
(Autonomous Institution affiliated to VTU, Belagavi)
Bengaluru – 19

Department of Computer Science and Engineering



Report on
“Verilog Programs using Structural Modeling, Behavioral
Modeling and Data Flow Modeling”


LOGIC DESIGN - 19CS3PCLOD

(Autonomous Scheme 2019)

Submitted by
Name: Khushil M Sindhwad
USN: 1BM19CS072

B.M.S. College of Engineering

 *(Autonomous Institution affiliated to VTU,
Belagavi)*
Bengaluru - 19
Department of Computer Science and Engineering



Certificate

This is to certify that Mr. **Khushil M Sindhwad** has satisfactorily completed the course of Experiments in **LOGIC DESIGN course** prescribed by the Department during the year **2020-2021**.

Name of the Candidate: Khushil M Sindhwad

USN No.: **1BM19CS072** Semester: **3rd**

Marks	
Max. Marks	Obtained
10	

Marks in Words	


Signature of the staff in-charge

Head of the Department

Date:

Verilog Program List

19CS3PCLOD

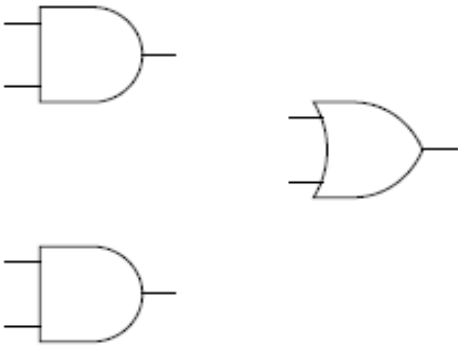Serial No.	Title
	CYCLE I Structural Modeling
•	<p>Write HDL implementation for the following Logic</p> <ul style="list-style-type: none"> • AND/OR/NOT <p>Simulate the same using structural model and depict the timing diagram for valid inputs.</p>
•	<p>Write HDL implementation for the following Logic</p> <ul style="list-style-type: none"> • NAND/NOR <p>Simulate the same using structural model and depict the timing diagram for valid inputs.</p>
•	<div style="display: flex; align-items: center; justify-content: center; gap: 20px;">  </div> <p>the following Logic</p> <p style="text-align: right;">Write HDL implementation for</p>

	Simulate the same using structural model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 4:1 Multiplexer. Simulate the same using structural model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 2-to-4 decoder. Simulate the same using structural model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 4-to-2 encoder. Simulate the same using structural model and depict the timing diagram for valid inputs.
	CYCLE II Behavior Modeling
•	Write HDL implementation for a RS flip-flop using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a JK flip-flop using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 4-bit right shift register using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 3-bit up-counter using behavioral model. Simulate the same using Behavior model and depict the timing diagram for valid inputs.
	CYCLE III Dataflow Modeling
•	Write HDL implementation for AND/OR/NOT gates using data flow model. Simulate the same using Dataflow model and depict the timing diagram for valid inputs.
•	Write HDL implementation for a 3-bit full adder using data flow model. Simulate the same using Dataflow model and depict the timing diagram for valid inputs.

STRUCTURAL MODELING

Experiment 1

- Write HDL implementation for the following Logic
 - AND/OR/NOT

Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (andornot.v)


```
module andornot(a,b,y);  
    input a,b;  
    output [2:0]y;  
    and an(y[2],a,b);  
    or o(y[1],a,b);  
    not nt(y[0],a);  
  
endmodule
```

TESTBENCH MODULE (andornot_tb.v)

```
`include "andornot.v"  
module andornot_tb;  
    reg A,B;  
    wire [2:0]y;  
    andornot ob(A,B,y);  
    initial  
    begin  
        $dumpfile("test.vcd");  
        $dumpvars(0,andornot_tb);  
        A=1'b0;  
        B=1'b0;  
        #20  
        A=1'b0;  
        B=1'b1;  
        #20  
        A=1'b1;  
        B=1'b0;  
        #20  
        A=1'b1;  
        B=1'b1;  
        #20  
        $finish;  
    end  
endmodule
```

```
Command Prompt
Microsoft Windows [Version 10.0.18363.1379]
(c) 2019 Microsoft Corporation. All rights reserved.

C:\Users\khush>cd ..
C:\Users>cd..
C:\>cd..
C:\>cd iverilog/bin/andornot
C:\iverilog\bin\andornot>iverilog -o andornot_tb.vvp andornot_tb.v
C:\iverilog\bin\andornot>vvp andornot_tb.vvp
VCD info: dumpfile test.vcd opened for output.
andornot_tb.v:22: $finish called at 80 (1s)
C:\iverilog\bin\andornot>gtkwave test.vcd
GTKWave Analyzer v3.3.108 (w)1999-2020 BSI
[0] start time.
[80] end time.
WM Destroy
C:\iverilog\bin\andornot>
```

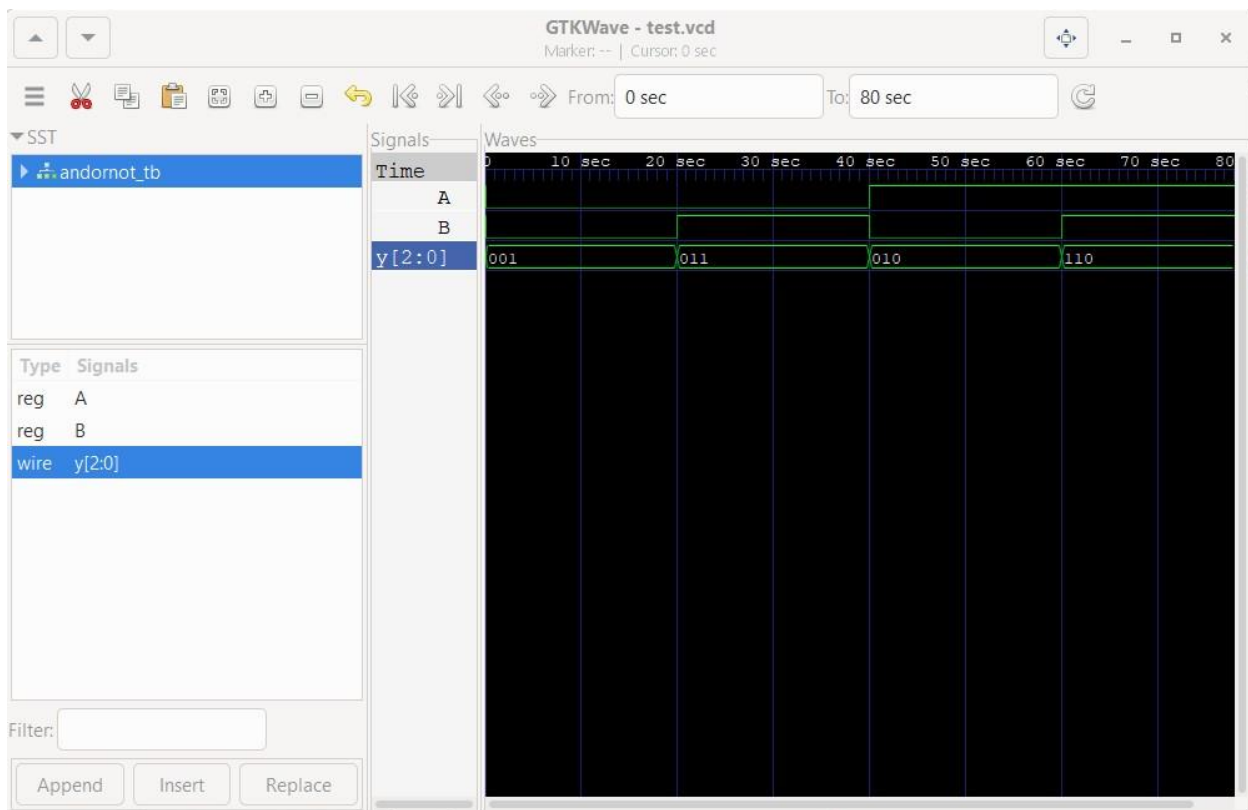

Experiment 2

Write HDL implementation for the following Logic

- NAND/NOR

Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (nandnor.v)

```
module nandnor(a,b,y);  
    input a,b;  
    output [1:0]y;  
    nand na(y[1],a,b);  
    nor no(y[0],a,b);  
endmodule
```

TEST MODULE (tb_nandnor.v)

```
`include "nandnor.v"  
module tb_nandnor;  
    reg a,b;  
    wire [1:0]y;  
    nandnor ob(a,b,y);  
    initial  
    begin  
        $dumpfile("nandnor.vcd");  
        $dumpvars(0,tb_nandnor);  
        a=1'b0;b=1'b0;  
        #20  
        a=1'b0;b=1'b1;  
        #20  
        a=1'b1;b=1'b0;  
        #20  
        a=1'b1;b=1'b1;  
        #20  
        $finish;  
    end  
endmodule
```

```
Command Prompt
C:\Users\khush>cd C:\iverilog\bin\nandnor\

C:\iverilog\bin\nandnor>iverilog -o nandnor.vvp nandnor.v

C:\iverilog\bin\nandnor>vvp nandnor.vvp

C:\iverilog\bin\nandnor>iverilog -o nandnor.vvp tb_nandnor.v
tb_nandnor.v:5: error: Unknown module type: s_nandnor
2 error(s) during elaboration.
*** These modules were missing:
    s_nandnor referenced 1 times.
***

C:\iverilog\bin\nandnor>iverilog -o nandnor.vvp tb_nandnor.v


C:\iverilog\bin\nandnor>vvp nandnor.vvp
VCD info: dumpfile nandnor.vcd opened for output.
tb_nandnor.v:18: $finish called at 80 (1s)

C:\iverilog\bin\nandnor>gtkwave nandnor.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI


[0] start time.
[80] end time.
WM Destroy

C:\iverilog\bin\nandnor>
```

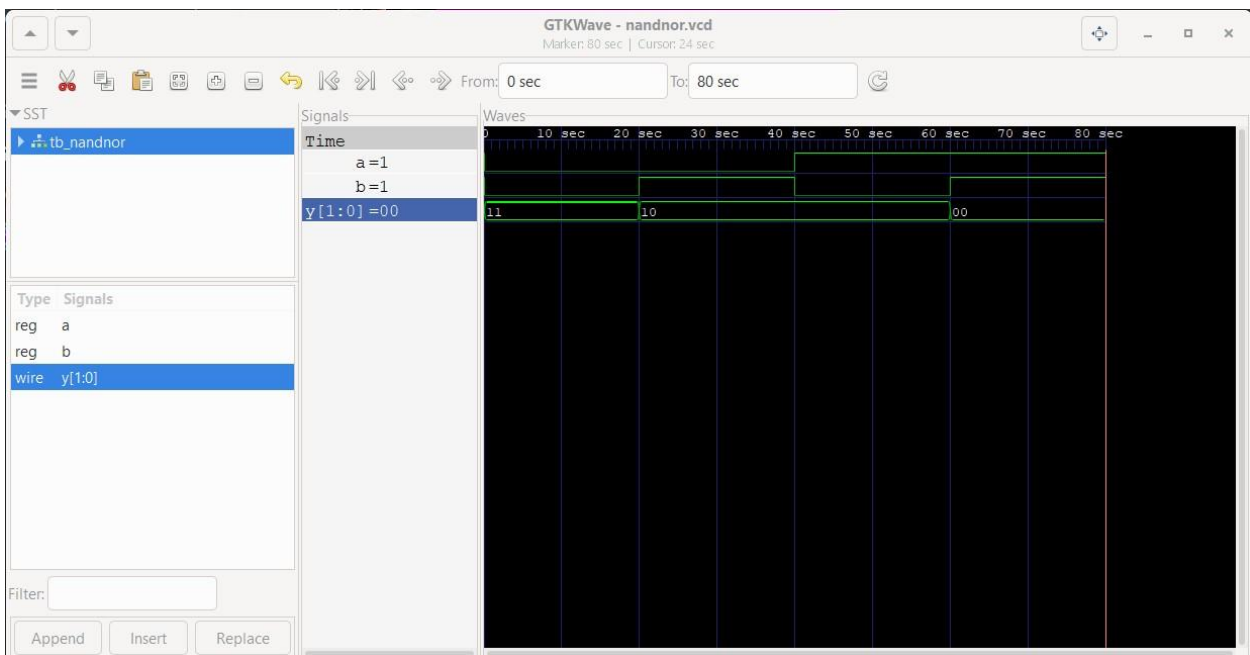

Experiment 3

 Write HDL implementation for the following Logic



Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (andor.v)

```
module andor(A,B,C,D,Y);
input A,B,C,D;
output Y;
wire a1,a2;
and g1(a1,A,B);
and g2(a2,C,D);
or g3(Y,a1,a2);
endmodule
```

TEST MODULE (tb_andor.v)

```
`include "andor.v"
module tb_andor;
reg a,b,c,d;
wire y;
andor ao(a,b,c,d,y);
initial
begin
$dumpfile("andor.vcd");
$dumpvars(0,tb_andor);
a=0; b=1; c=1; d=1; #10
a=0; b=0; c=1; d=0; #10
$finish;
end
endmodule
```

```
Command Prompt - gtkwave andor.vcd

MM Destroy

C:\iverilog\bin\andor>iverilog andor.v


C:\iverilog\bin\andor>iverilog -o andor.vvp tb_andor.v

C:\iverilog\bin\andor>vvp andor.vvp
VCD info: dumpfile andor.vcd opened for output.
tb_andor.v:12: $finish called at 20 (1s)

C:\iverilog\bin\andor>gtkwave andor.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[20] end time.
```

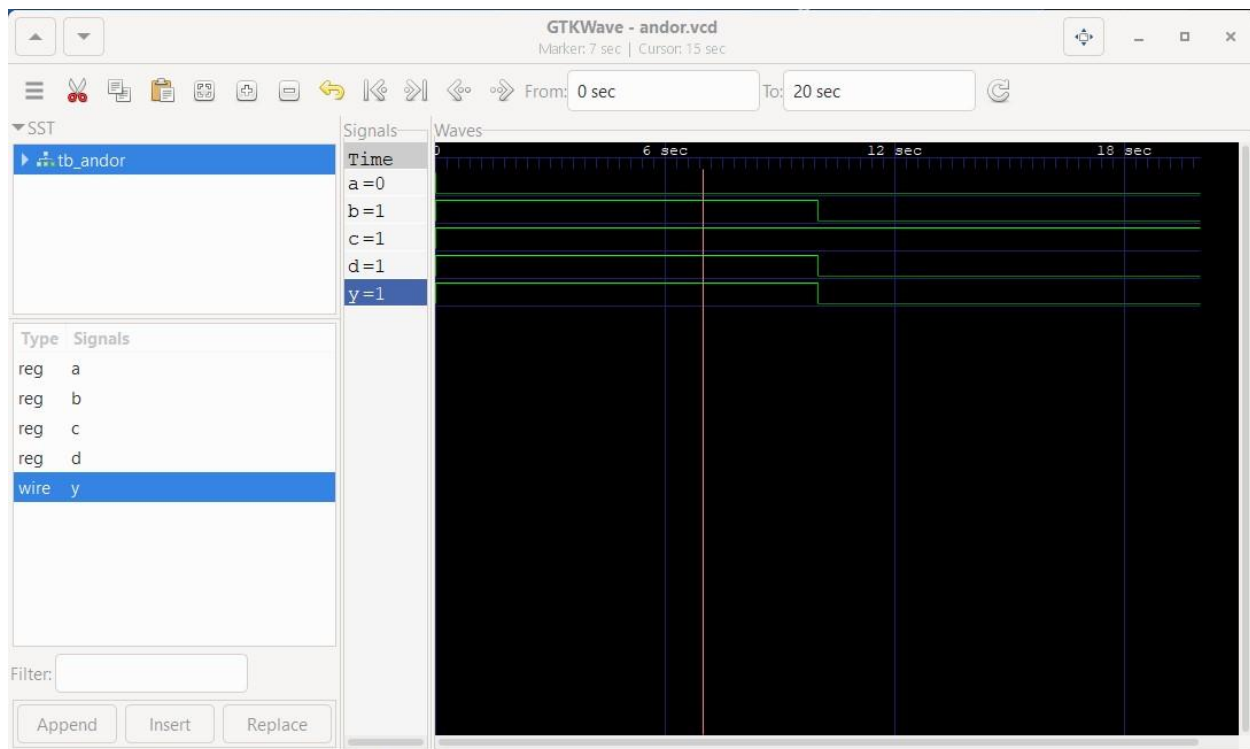

Experiment 4

Write HDL implementation for a 4:1 Multiplexer. Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (mux4to1.v)

```
module mux4to1(a, b, c, d, sel1, sel2, y);  
    input a, b, c, d, sel1, sel2;  
    output y;  
    wire and1, and2, and3, and4;  
    and g1(and1, a, ~sel1, ~sel2);  
    and g2(and2, b, ~sel1, sel2);  
    and g3(and3, c, sel1, ~sel2);  
    and g4(and4, d, sel1, sel2);  
    or g5(y, and1, and2, and3, and4);  
  
endmodule
```

TESTBENCH MODULE (tb_mux4to1.v)

```
`include "mux4to1.v"  
module tb_mux4to1;  
    reg a, b, c, d, sel1, sel2;  
    wire y;  
    mux4to1 mg(a, b, c, d, sel1, sel2, y);  
    initial  
    begin  
        $dumpfile("mux4to1.vcd");  
        $dumpvars(0, tb_mux4to1);  
        a = 0; b = 0; c = 0; d = 0; sel1 = 0; sel2 = 0;  
        #20  
        a = 1; b = 0; c = 0; d = 0; sel1 = 0; sel2 = 0;  
        #20  
        a = 0; b = 0; c = 0; d = 0; sel1 = 0; sel2 = 1;  
        #20  
        a = 0; b = 1; c = 0; d = 0; sel1 = 0; sel2 = 1;  
        #20  
    end  
endmodule
```

```
a = 0; b = 0; c = 0; d = 0; sel1 = 1; sel2 = 0;  
#20  
a = 0; b = 0; c = 1; d = 0; sel1 = 1; sel2 = 0;  
#20  
a = 0; b = 0; c = 0; d = 0; sel1 = 1; sel2 = 1;  
#20  
a = 0; b = 0; c = 0; d = 1; sel1 = 1; sel2 = 1;  
#20  
$finish;  
end
```

```
endmodule
```

```
Command Prompt - gtkwave mux4to1.vcd
C:\iverilog\bin\andor>
C:\iverilog\bin\andor>cd C:\iverilog\bin\4_1_muxplexer\

C:\iverilog\bin\4_1_muxplexer>iverilog mux4to1.v


C:\iverilog\bin\4_1_muxplexer>iverilog -o mux4to1.vvp tb_mux4to1.v

C:\iverilog\bin\4_1_muxplexer>vvp mux4to1.vvp
VCD info: dumpfile mux4to1.vcd opened for output.
tb_mux4to1.v:26: $finish called at 160 (1s)

C:\iverilog\bin\4_1_muxplexer>gtkwave mux4to1.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[160] end time.
```

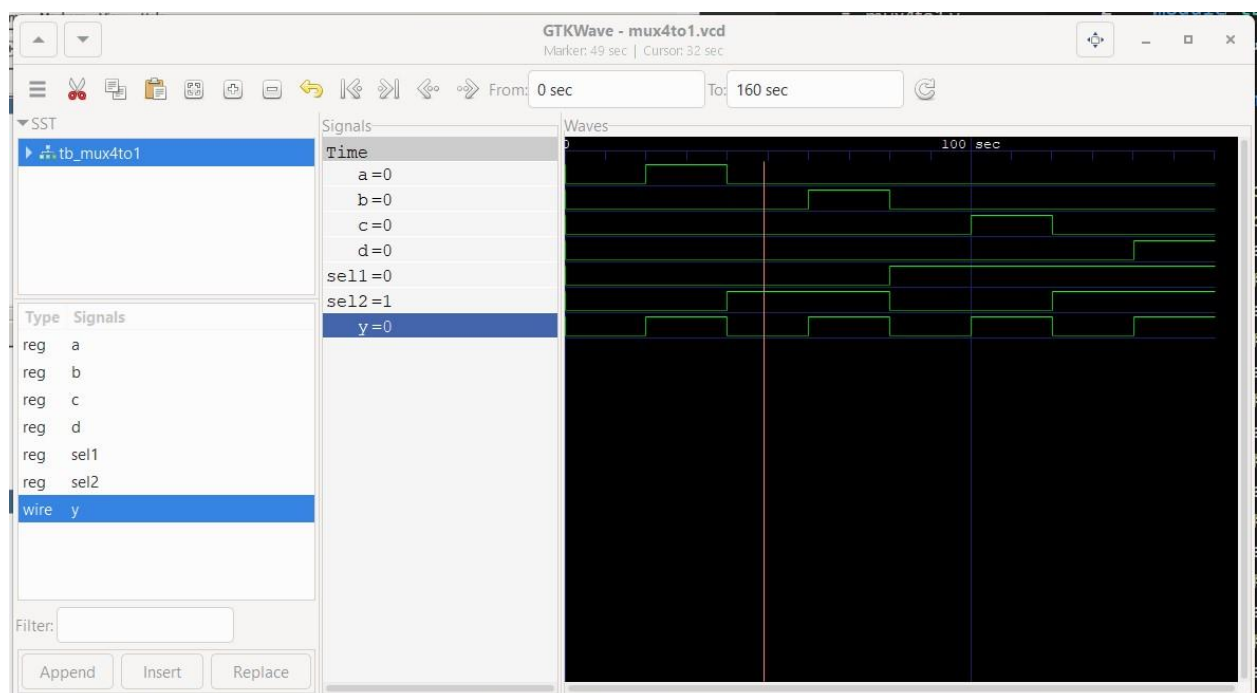

Experiment 5

Write HDL implementation for a 2-to-4 decoder. Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (decoder.v)

```
module decoder(Do,Din,En);
```

```
    input En;
```

```
    input[1:0]Din;
```

```
    output [3:0]Do;
```

```
    reg [3:0]Do;
```

```
    always@(En or Din)
```

```
    begin
```

```
        if(En)
```

```
        begin
```

```
            case(Din)
```

```
                2'b00:Do=4'b0001;
```

```
                2'b01:Do=4'b0010;
```

```
                2'b10:Do=4'b0100;
```

```
                2'b11:Do=4'b1000;
```

```
                default:Do=4'bzzzz;
```

```
            endcase
```

```
        end
```

```
    end
```

```
endmodule
```

TEST BENCH MODULE (tb_decoder.v)

```
`include "decoder.v"
```

```
module tb_decoder;
```

```
    reg [1:0]Din;
```

```
    reg En;
```

```
wire [3:0]Do;

decoder udue(.Do(Do),.Din(Din),.En(En));

initial begin

    $dumpfile("decoder.vcd");

    $dumpvars(0,tb_decoder);

    En=1;

    Din=2'b00;#100;

    Din=2'b01;#100;

    Din=2'b10;#100;

    Din=2'b11;#100;

end

endmodule
```

```
Command Prompt
C:\iverilog\bin\4_1_muxplexer>gtkwave mux4to1.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[160] end time.

C:\iverilog\bin\4_1_muxplexer>cd C:\iverilog\bin\4_to_2_encoder\decoder.v
The directory name is invalid.

C:\iverilog\bin\4_1_muxplexer>cd C:\iverilog\bin\4_to_2_encoder\

C:\iverilog\bin\4_to_2_encoder>cd C:\iverilog\bin\2_to_4_decoder\

C:\iverilog\bin\2_to_4_decoder>iverilog decoder.v

C:\iverilog\bin\2_to_4_decoder>iverilog -o decoder.vvp tb_decoder.v


C:\iverilog\bin\2_to_4_decoder>vvp decoder.vvp
VCD info: dumpfile decoder.vcd opened for output.

C:\iverilog\bin\2_to_4_decoder>gtkwave decoder.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[400] end time.
WM Destroy

C:\iverilog\bin\2_to_4_decoder>
```

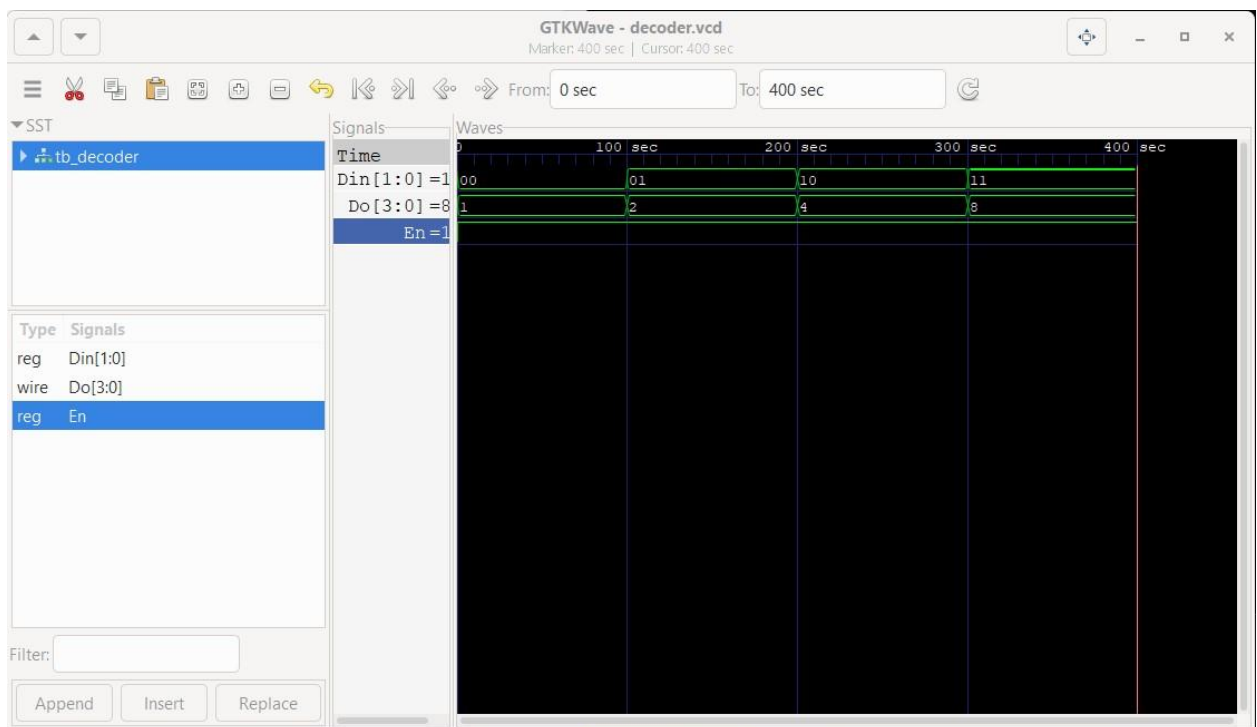

Experiment 6

Write HDL implementation for a 4-to-2 encoder. Simulate the same using structural model and depict the timing diagram for valid inputs.

MAIN MODULE (encoder.v)

```
module encoder(Do,Din,En);
input En;
input[3:0]Din;

output [1:0]Do;
reg [1:0]Do;
always@(En or Din)
begin
if(En)
begin
case(Din)
4'b0001:Do=2'b00;
4'b0010:Do=2'b01;
4'b0100:Do=2'b10;
4'b1000:Do=2'b11;
default:Do=2'bzz;
endcase
end
end
endmodule
```

TESTBENCH MODULE (tb_encoder.v)

```
`include "encoder.v"
module tb_encoder;
reg [3:0]Din;
reg En;
wire [1:0]Do;
encoder mux1(.Do(Do),.Din(Din),.En(En));
initial begin
$dumpfile("encoder.vcd");
$dumpvars(0,tb_encoder);
En=1;
Din=4'b0001;#100;
Din=4'b0010;#100;
Din=4'b0100;#100;
Din=4'b1000;#100;
end
endmodule
```

```
Command Prompt

C:\iverilog\bin\2_to_4_decoder>vvp decoder.vvp
VCD info: dumpfile decoder.vcd opened for output.

C:\iverilog\bin\2_to_4_decoder>gtkwave decoder.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[400] end time.
MM Destroy

C:\iverilog\bin\2_to_4_decoder>cd C:\iverilog\bin\4_to_2_encoder\

C:\iverilog\bin\4_to_2_encoder>iverilog encoder.v

C:\iverilog\bin\4_to_2_encoder>iverilog -o encoder.vvp tb_encoder.v


C:\iverilog\bin\4_to_2_encoder>vvp encoder.vvp
VCD info: dumpfile encoder.vcd opened for output.

C:\iverilog\bin\4_to_2_encoder>gtkwave encoder.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[400] end time.
MM Destroy

C:\iverilog\bin\4_to_2_encoder>
```

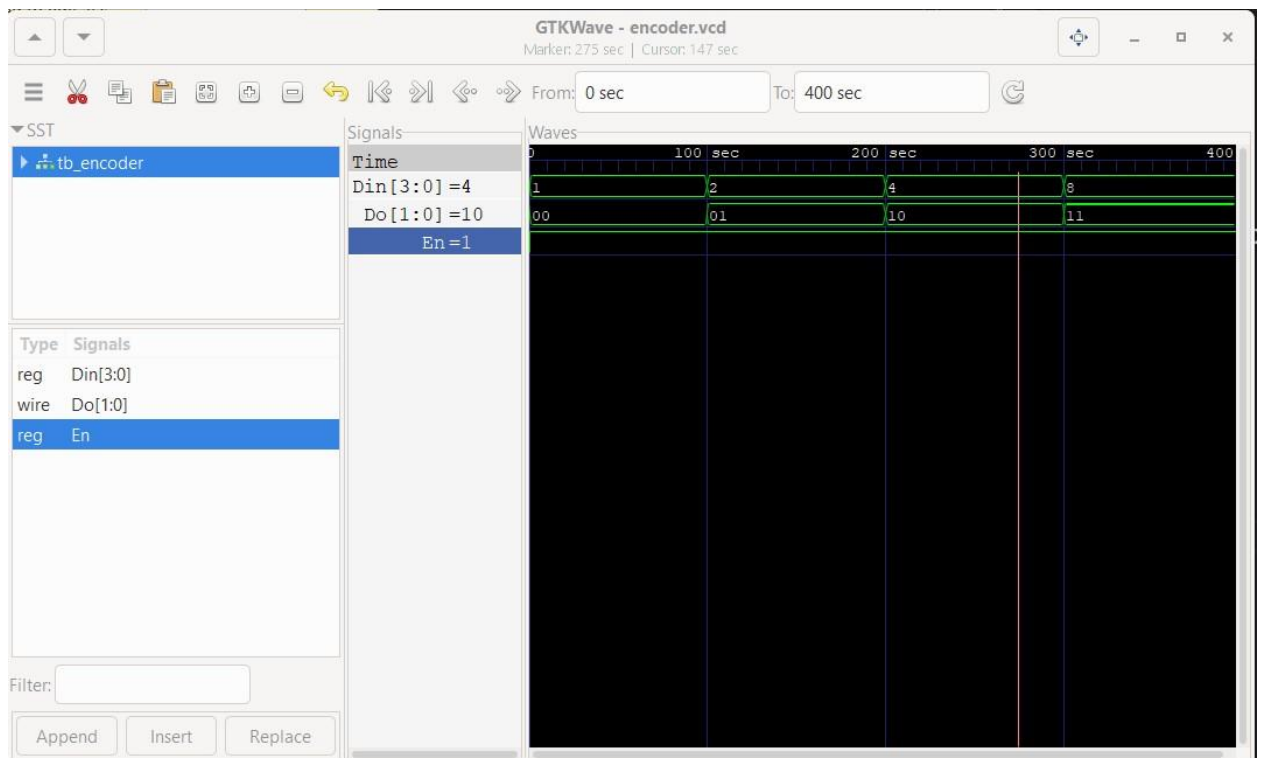

BEHAVIOR MODELING

Experiment 7

Write HDL implementation for a SR flip-flop using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE (SR_FF.v)

```
module SR_FF (sr, clk, q, qb);
input [1:0] sr;
input clk;
output reg q=1'b0;
output reg qb;
always @ (posedge clk)
begin
    case (sr)
        2'b00 : q = q ;
        2'b01 : q = 1'b0 ;
        2'b10 : q = 1'b1 ;
        2'b11 : q = 1'bz ;
    endcase
    qb =~ q;
end
endmodule
```

TEST MODULE (tb_SR_FF.v)

```
`include "SR_FF.v"
module tb_SR_FF;
    reg [1:0] A;
    reg c;
    wire x, xb;
    SR_FF srff(A,c,x,xb);
    initial c=1'b0;
    always #5 c=~c;
    initial
    begin
        $dumpfile("srff.vcd");
        $dumpvars(0,tb_SR_FF);

        A=2'b00; #10
        A=2'b01;#10
        A=2'b10;#10
        A=2'b11;
        #20 $finish;
    end
endmodule
```

```
C:\windows\system32\cmd.exe - gtkwave srff.vcd
Microsoft Windows [Version 10.0.18363.1379]
(c) 2019 Microsoft Corporation. All rights reserved.

C:\Users\khush>cd C:\iverilog\bin\SRFF\

C:\iverilog\bin\SRFF>iverilog SR_FF.v

C:\iverilog\bin\SRFF>iverilog -o srff.vvp tb_SR_FF.v

C:\iverilog\bin\SRFF>vvp srff.vvp
tb_SR_FF.v:16: $finish called at 50 (1s)

C:\iverilog\bin\SRFF>iverilog SR_FF.v


C:\iverilog\bin\SRFF>iverilog -o srff.vvp tb_SR_FF.v

C:\iverilog\bin\SRFF>vvp srff.vvp
VCD info: dumpfile srff.vcd opened for output.
tb_SR_FF.v:18: $finish called at 50 (1s)

C:\iverilog\bin\SRFF>gtkwave srff.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[50] end time.
```

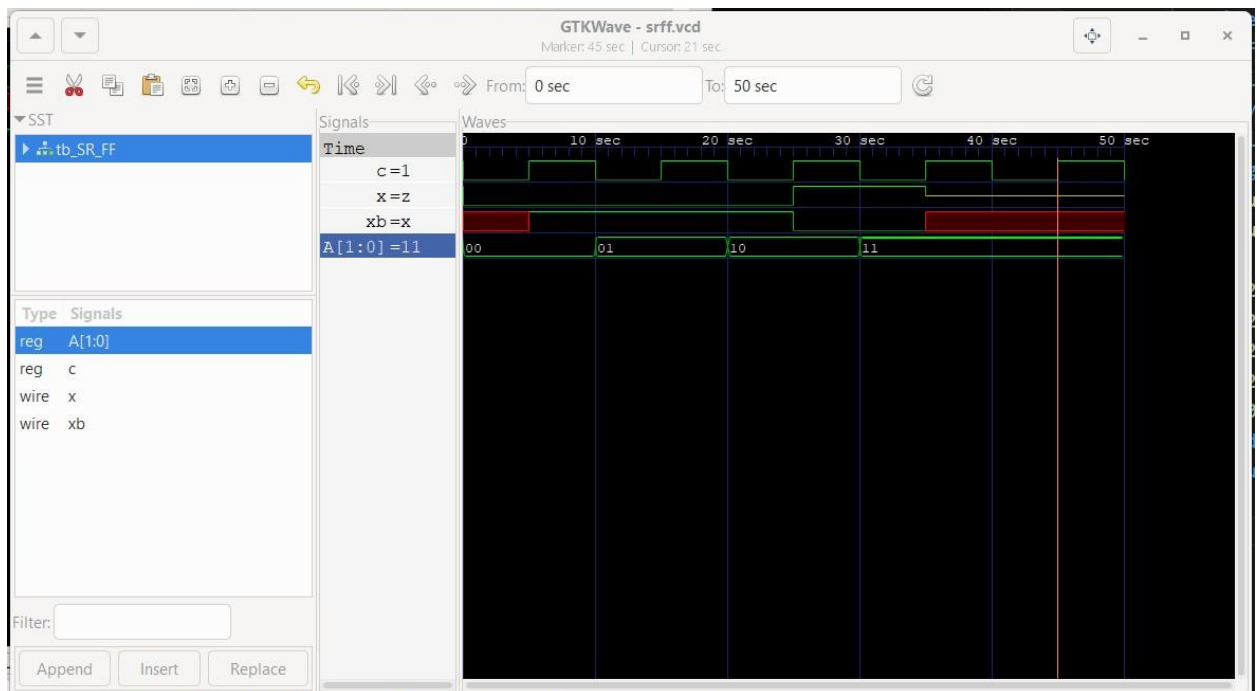

Experiment 8

Write HDL implementation for a JK flip-flop using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE (JK_FF.v)

```
module JK_FF(j,k,clk,reset,q,q_bar);
input j,k,clk,reset;
output q,q_bar;
wire j,k,clk,reset;
reg q,q_bar;

always@(posedge clk)begin

if(reset)begin
q=1'b0;
q_bar=1'b1;

end else begin

case({j,k})
{1'b0,1'b0}:begin q=q;q_bar=q_bar;end
{1'b0,1'b1}:begin q=1'b0;q_bar=1'b1;end
{1'b1,1'b0}:begin q=1'b1;q_bar=1'b0;end
{1'b1,1'b1}:begin q=~q;q_bar=~q_bar;end
endcase
end
end
endmodule
```

TEST MODULE (tb_JK_FF.v)

```
`include "JK_FF.v"
module tb_JK_FF;
reg clk;
reg reset;
reg j,k;
wire q;
wire qb;
JK_FF flipflop(.clk(clk),.reset(reset),.j(j),.k(k),.q(q),.q_bar(qb));
initial begin
$dumpfile("jkff.vcd");
$dumppvars(0,tb_JK_FF);
$monitor(clk,j,k,q,qb,reset);
j=1'b0;
k=1'b0;
reset=1;
clk=1;
#100
reset=0;
j=1'b1;
k=1'b0;
```

```
#100
reset=0;
j=1'b0;
k=1'b1;
#100
reset=0;
j=1'b1;
k=1'b1;
#100
reset=0;
j=1'b0;
k=1'b0;
#100
reset=1;$finish;
end
endmodule
```

```
C:\windows\system32\cmd.exe

C:\iverilog\bin\JKFF>iverilog JK_FF.v

C:\iverilog\bin\JKFF>iverilog tb_JK_FF.v

C:\iverilog\bin\JKFF>iverilog -o jkff.vvp tb_JK_FF.v


C:\iverilog\bin\JKFF>vvp jkff.vvp
VCD info: dumpfile jkff.vcd opened for output.
100011
110010
101010
111010
100010
tb_JK_FF.v:34: $finish called at 500 (1s)
100011

C:\iverilog\bin\JKFF>gtkwave jkff.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[500] end time.
WM Destroy

C:\iverilog\bin\JKFF>
```

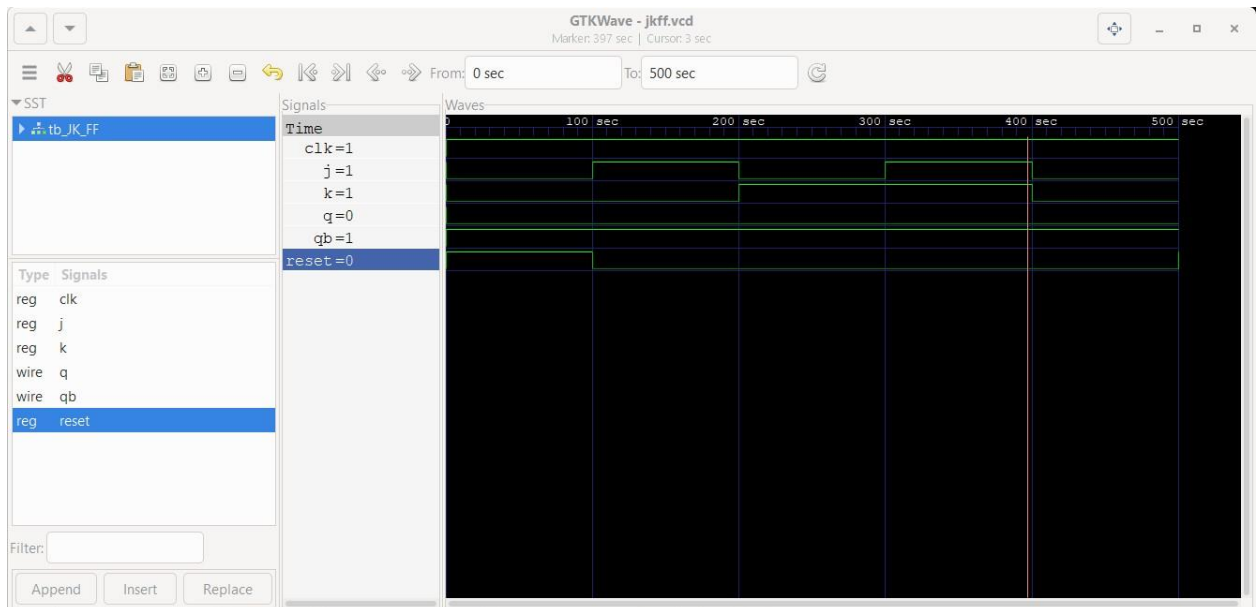

Experiment 9

Write HDL implementation for a 4-bit right shift register using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

MAIN MODULE (rshiftreg.v)

```
module rshiftreg(input clk,input clrb,input sdr,output reg [3:0]q);
always @(posedge(clk),negedge(clrb))
if(~clrb)
q<=4'b0000;
else
q<={sdr,q[3:1]};
endmodule
```

TEST MODULE (tb_rshiftreg.v)

```
`include "rshiftreg.v"

module tb_rshiftreg;

reg clk,clrb,sdr;

wire [3:0]q;

rshiftreg rs(clk,clrb,sdr,q);

initial

begin

$dumpfile("shift.vcd");

$dumpvars(0,tb_rshiftreg);

clk=1;

clrb=0;

sdr=1;

#100

clrb=1;

sdr=1;

#150

sdr=0;

#200
```


\$finish;

end

always #5 clk=~clk;

endmodule

```

C:\windows\system32\cmd.exe

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[500] end time.
WM Destroy

C:\iverilog\bin\JKFF>cd C:\iverilog\bin\4bitShiftRegister\

C:\iverilog\bin\4bitShiftRegister>iverilog rshiftreg.v
rshiftreg.v: No such file or directory
No top level modules, and no -s option.

C:\iverilog\bin\4bitShiftRegister>iverilog rshiftreg.v

C:\iverilog\bin\4bitShiftRegister>iverilog -o rshift.vvp tb_rshiftreg.v

C:\iverilog\bin\4bitShiftRegister>vvp rshift.vvp
VCD info: dumpfile shift.vcd opened for output.
tb_rshiftreg.v:19: $finish called at 450 (1s)


C:\iverilog\bin\4bitShiftRegister>gtkwave shift.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[450] end time.
WM Destroy

C:\iverilog\bin\4bitShiftRegister>

```

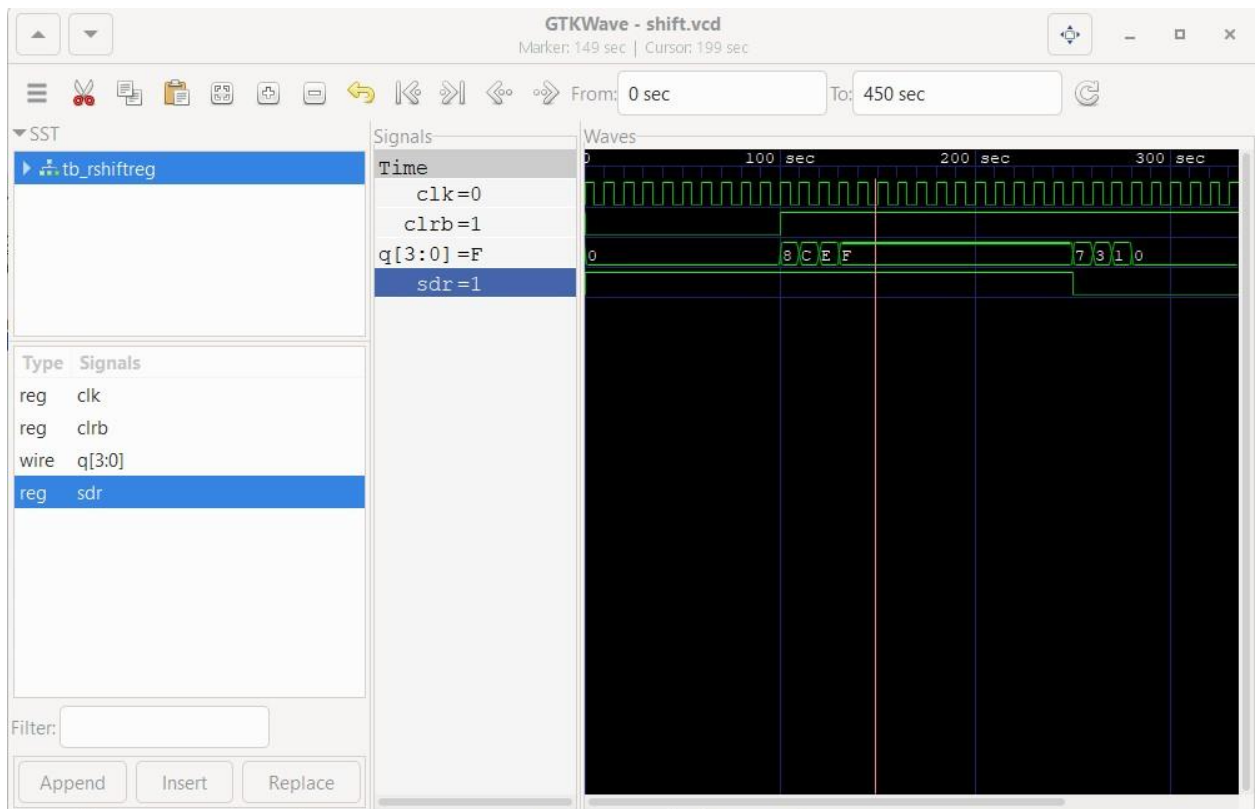

Experiment 10

Write HDL implementation for a 3-bit up-counter using behavioral model. Simulate the same using behavioral model and depict the timing diagram for valid inputs.

Main Module (upcounter.v)

```
module upcounter( count,rst,clk);
input rst, clk;
output reg [2:0] count;
always @(posedge (clk))
if (rst)
count<= 3'b000;
else
count<= count + 1;
endmodule
```

TEST MODULE (tb_upcounter.v)

```
`include "upcounter.v"
module tb_upcounter;
reg r,c;
wire [2:0] ct;

upcounter countbeh (ct,r,c);
initial
begin
$dumpfile("count.vcd");
$dumpvars(0,tb_upcounter);
r =1;
c=0;
#100 r=0;
#200 $finish;
end
always #5 c=~c;
endmodule
```

```
C:\windows\system32\cmd.exe
C:\iverilog\bin\3bitUpCounter>dir
Volume in drive C is Windows
Volume Serial Number is 5462-9D62

Directory of C:\iverilog\bin\3bitUpCounter

22-02-2021  15:00    <DIR>          .
22-02-2021  15:00    <DIR>          ..
22-02-2021  15:01                265 tb_upcounter.v
22-02-2021  14:59                166 upcounter.v
                2 File(s)          431 bytes
                2 Dir(s) 106,920,423,424 bytes free

C:\iverilog\bin\3bitUpCounter>iverilog upcounter.v

C:\iverilog\bin\3bitUpCounter>iverilog -o counter.vvp tb_upcounter.v


C:\iverilog\bin\3bitUpCounter>vvp counter.vvp
VCD info: dumpfile count.vcd opened for output.
tb_upcounter.v:14: $finish called at 300 (1s)

C:\iverilog\bin\3bitUpCounter>gtkwave count.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[300] end time.
WM Destroy

C:\iverilog\bin\3bitUpCounter>
```

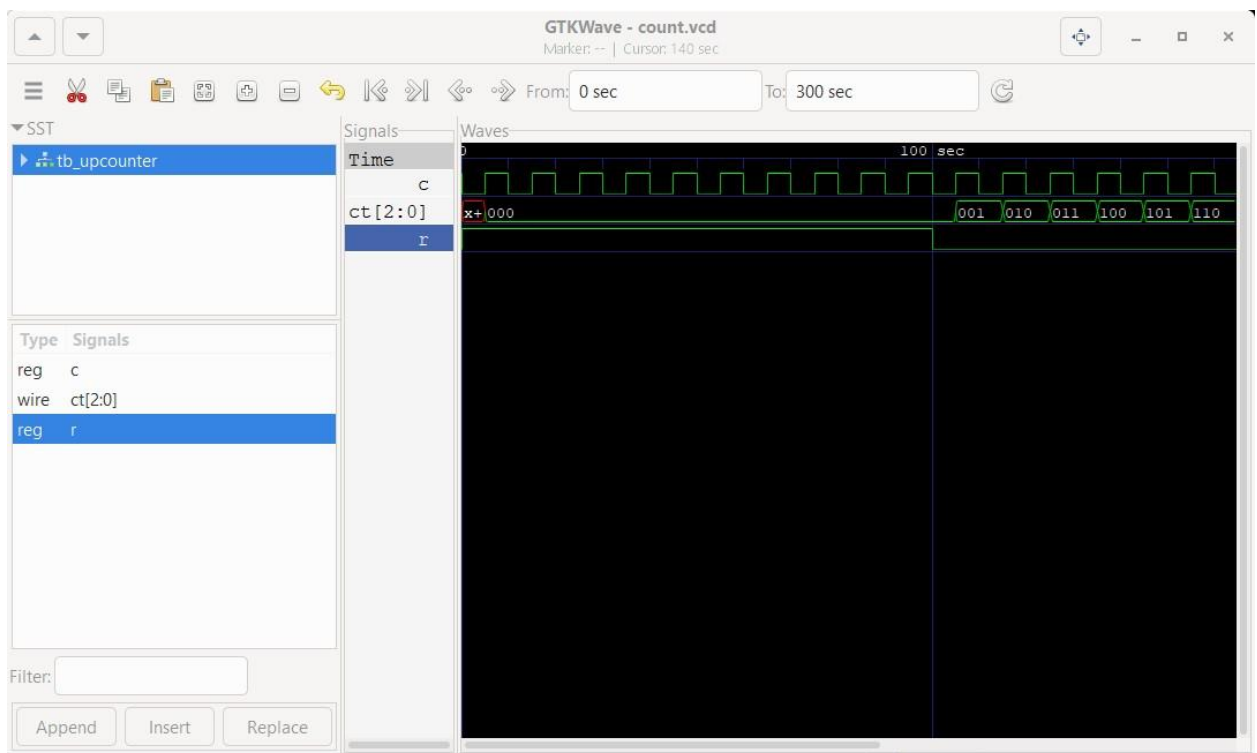

DATA FLOW MODELING

Experiment 11

Write HDL implementation for AND/OR/NOT gates using data flow model. Simulate the same using data flow model and depict the timing diagram for valid inputs.

MAIN MODULE (andornot.v)

```
module andornot(input a,b,output [2:0]y);  
  
    assign y[2]=a&b;  
  
    assign y[1]=a|b;  
  
    assign y[0]=~a;  
  
endmodule
```

TESTBENCH MODULE (tb_andornot.v)

```
`include "andornot.v"  
  
module tb_andornot;  
  
    wire [2:0]y;  
  
    reg a,b;  
  
    andornot dut(.y(y),.a(a),.b(b));  
  
    initial  
  
    begin  
  
        $dumpfile("andornot.vcd");  
  
        $dumpvars(0,tb_andornot);  
  
        a=1'b0;  
  
        b=1'b0;  
  
        #50;  
  
        a=1'b0;  
  
        b=1'b1;  
  
        #50;  
  
        a=1'b1;  
  
        b=1'b0;
```

#50;

a=1'b1;


b=1'b1;

#50;

end

endmodule

```
C:\windows\system32\cmd.exe - gtkwave andornot.vcd
C:\iverilog\bin\3bitUpCounter>iverilog -o counter.vvp tb_upcounter.v
C:\iverilog\bin\3bitUpCounter>vvp counter.vvp
VCD info: dumpfile count.vcd opened for output.
tb_upcounter.v:14: $finish called at 300 (1s)
C:\iverilog\bin\3bitUpCounter>gtkwave count.vcd
GTKWave Analyzer v3.3.108 (w)1999-2020 BSI
[0] start time.
[300] end time.
WM Destroy
C:\iverilog\bin\3bitUpCounter>cd C:\iverilog\bin\andornot_dataflow\
C:\iverilog\bin\andornot_dataflow>iverilog andornot.v
C:\iverilog\bin\andornot_dataflow>iverilog -o andornot.vvp tb_andornot.v
C:\iverilog\bin\andornot_dataflow>vvp andornot.vvp
VCD info: dumpfile andornot.vcd opened for output.
C:\iverilog\bin\andornot_dataflow>gtkwave andornot.vcd
GTKWave Analyzer v3.3.108 (w)1999-2020 BSI
[0] start time.
[200] end time.
```

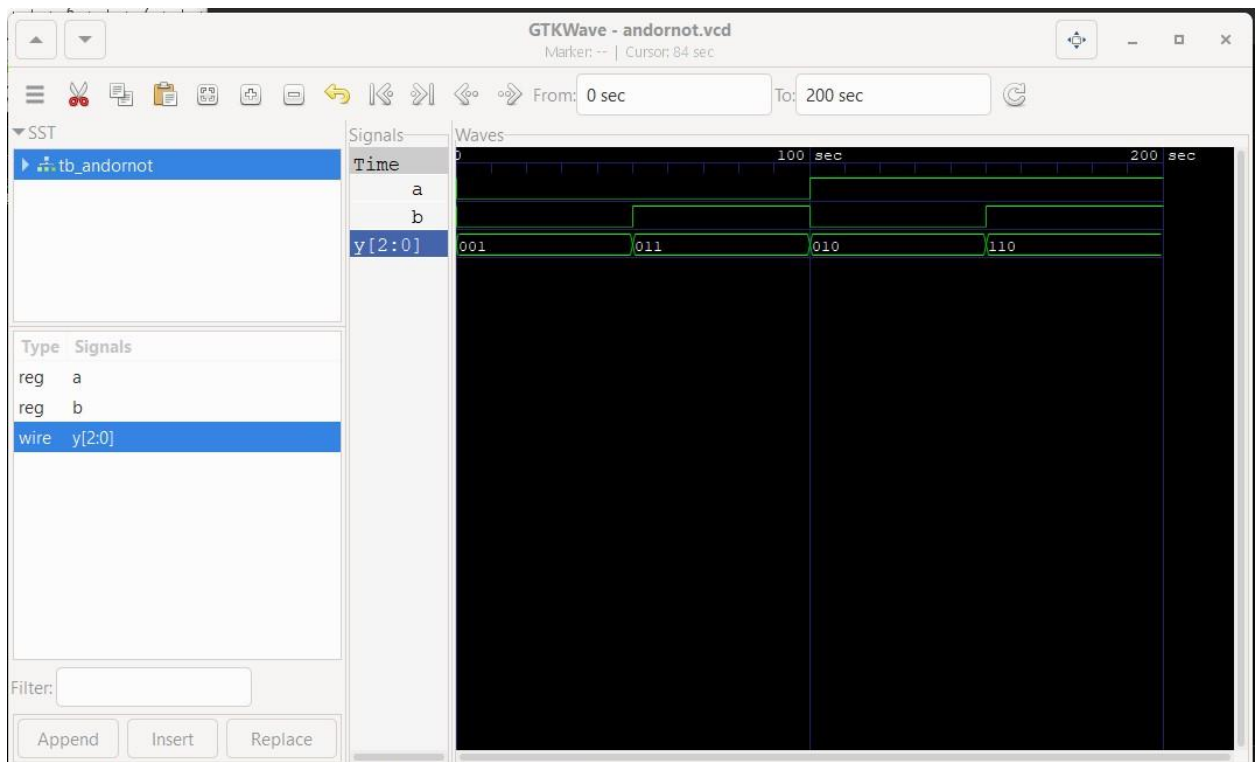

Experiment 12

Write HDL implementation for a 3-bit full adder using data flow model. Simulate the same using data flow model and depict the timing diagram for valid inputs.

MAIN MODULE (fulladder.v)

```
module fulladder(a,b,cin,s,cout);  
input a,b,cin;  
output s,cout;  
assign s=a^b^cin;  
assign cout=(a&b)|(b&cin)|(cin&a);  
endmodule
```

TEST MODULE (tb_fulladder.v)

```
`include "fulladder.v"  
module tb_fulladder;  
reg a,b,cin;  
wire s,cout;  
fulladder f1(a,b,cin,s,cout);  
initial  
begin  
$dumpfile("fa.vcd");  
$dumpvars(0,tb_fulladder);  
a=1;b=1;cin=0;  
#5  
a=1;b=1;cin=1;  
#5  
a=0;b=1;cin=0;  
#100 $finish;  
end  
endmodule
```



```
C:\windows\system32\cmd.exe

[0] start time.
[110] end time.
WM Destroy

C:\iverilog\bin\fullAdder_dataflow>iverilog fulladder.v

C:\iverilog\bin\fullAdder_dataflow>iverilog -o fulladder.vvp tb_fulladder.v


C:\iverilog\bin\fullAdder_dataflow>vvp fulladder.vvp
VCD info: dumpfile fa.vcd opened for output.
tb_fulladder.v:15: $finish called at 110 (1s)

C:\iverilog\bin\fullAdder_dataflow>gtkwave fa.vcd

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.
[110] end time.
WM Destroy

C:\iverilog\bin\fullAdder_dataflow>
```

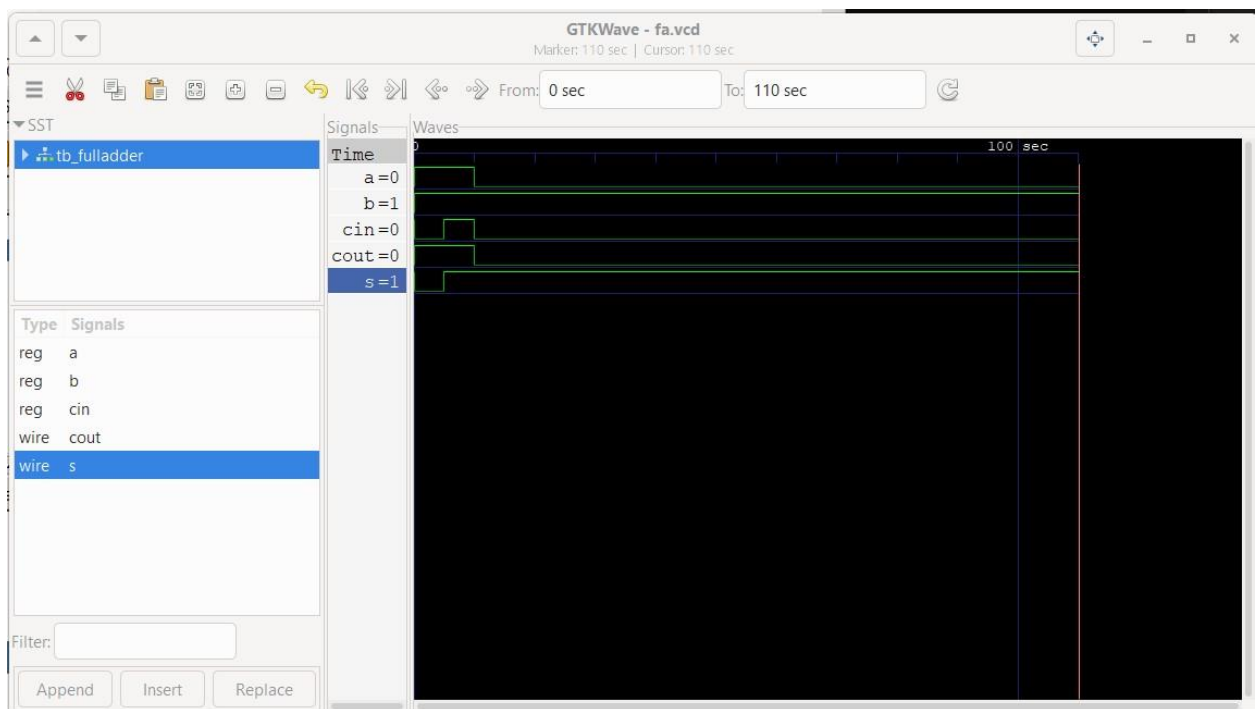

Signature of the staff in-charge